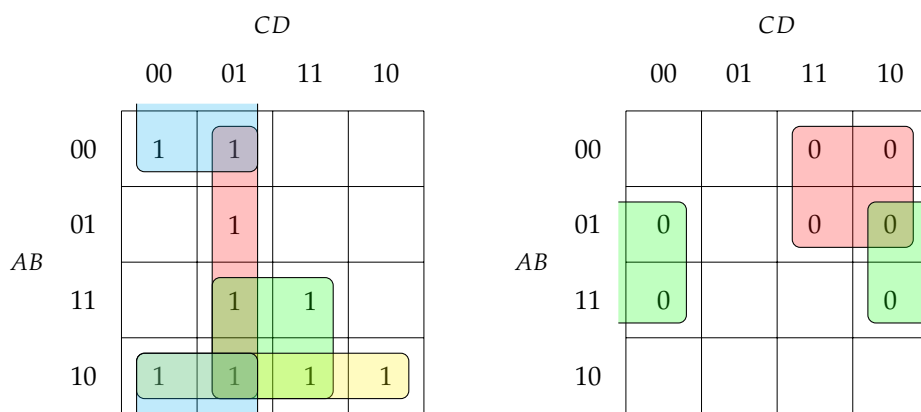


Assignment 3

1 DIGITAL DESIGN THEORY

Q. 1



(a) $F(A, B, C, D) = B'C' + C'D + AD + AB'$

(b) $F(A, B, C, D) = (B + C)' + (C + D')' + (A' + D')' + (A' + B)'$

(c) $F(A, B, C, D) = ((B'C')'(C'D)')(AD)'(AB')'$

(d) $F(A, B, C, D) = (B' + D)(A + C')$

(e) $F(A, B, C, D) = ((B' + D)' + (A + C')')'$

(f) $F(A, B, C, D) = (BD')'(A'C)'$

Q. 2


Four-bit Parity Generator

Input 4-bit message				Odd parity generator
A	B	C	D	P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0

1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

		CD			
		00	01	11	10
AB	00	1		1	
	01		1		1
	11	1		1	
	10		1		1

$$\begin{aligned}
 F(A, B, C, D) &= A'B'C'D' + A'B'CD + A'BC'D + A'BCD' + ABC'D' + ABCD + AB'C'D + AB'CD' \\
 &= A'D'(BC + B'C') + A'D(B'C + BC') + AD'(BC' + B'C) + AD(BC + B'C') \\
 &= A'D'(B \oplus C)' + A'D(B \oplus C) + AD'(B \oplus C) + AD(B \oplus C)' \\
 &= (A'D' + AD)(B \oplus C)' + (A'D + AD')(B \oplus C) \\
 &= (A \oplus D)'(B \oplus C)' + (A \oplus D)(B \oplus C) \\
 &= ((A \oplus D) \oplus (B \oplus C))'
 \end{aligned}$$

 


Three-bit Parity Checker

Input (3+1)-bit				Odd parity checker
A	B	C	P	C_P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0

0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

		<i>CP</i>			
		00	01	11	10
<i>AB</i>	00	1		1	
	01		1		1
	11	1		1	
	10		1		1

$$\begin{aligned}
 F(A, B, C, P) &= A'B'C'P' + A'B'CP + A'BC'P + A'BCP' + ABC'P' + ABCP + AB'C'P + AB'CP' \\
 &= A'P'(BC + B'C') + A'P(B'C + BC') + AP'(BC' + B'C) + AP(BC + B'C') \\
 &= A'P'(B \oplus C)' + A'P(B \oplus C) + AP'(B \oplus C) + AP(B \oplus C)' \\
 &= (A'P' + AP)(B \oplus C)' + (A'P + AP')(B \oplus C) \\
 &= (A \oplus P)'(B \oplus C)' + (A \oplus P)(B \oplus C) \\
 &= ((A \oplus P) \oplus (B \oplus C))'
 \end{aligned}$$

 

Q. 3

Input			Output		
x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0


		<i>xy</i>			
		00	01	11	10
<i>z</i>	0		1	1	
	1		1	1	1

		<i>xy</i>			
		00	01	11	10
<i>z</i>	0	1			1
	1	1		1	

		<i>xy</i>			
		00	01	11	10
<i>z</i>	0			1	1
	1	1	1		

$$A = y + xz$$
 
$$\begin{aligned} B &= x'y' + y'z' + xyz \\ &= (x' + z')y' + (xz)y \\ &= (xz)'y' + (xz)y \\ &= ((xz) \oplus y)' \\ C &= xz' + x'z \\ &= x \oplus z \end{aligned}$$



Q. 4


			A_2	A_1	A_0
\times			B_2	B_1	B_0
			A_2B_0	A_1B_0	A_0B_0
			A_2B_1	A_1B_1	A_0B_1
			A_2B_2	A_1B_2	A_0B_2
C_5	C_4	C_3	C_2	C_1	C_0

Starting with the traditional vertical multiplication, we found out that: ① a 3-bit multiplication is made up of three partial products; ② each partial product, is a 1-bit \times 3-bit, while bits can only be 0 or 1, this multiplication doesn't have carry out, and thus can simply use three; *and gate* to denote them ③ the partial products are added up to give the final result. Formally, we say:

$$\begin{aligned} C_0 &= A_0B_0 && \text{(no carry out)} \\ \{\text{Carry}_1, C_1\} &= A_1B_0 + A_0B_1 && \text{LHS} = 2 \times \text{Carry}_1 + C_1 \\ \{\text{Carry}_2, C_2\} &= A_2B_0 + A_1B_1 + A_0B_2 + \text{Carry}_1 \\ &\dots \\ \{\text{Carry}_4, C_4\} &= A_2B_2 + \text{Carry}_3 \\ C_5 &= \text{Carry}_4 \end{aligned}$$

A.k.a., since multiply takes *AND* operation of the all binary combination from the bits of A and B and add the result with shifting $i+j$ (i, j denotes the indices of bits in A and B) operations. To express the final result

 in binary form, we only take the least bit of output sum and feed the rest bits of output sum together with the carry out bit into the augend input of the next full adder.



The circuit can be represented as the following logic formulas:

$$C_0 = A_0 B_0$$

$$C_1 = (A_1 B_0) \oplus (A_0 B_1)$$

$$C_2 = (A_2 B_0) \oplus (A_1 B_1) \oplus (A_0 B_2) \oplus (A_1 B_0 A_0 B_1)$$

$$C_3 = (A_2 B_1) \oplus (A_1 B_2) \oplus (A_2 B_0 A_1 B_1 A_0 B_2 B_0)$$

$$C_4 = (A_2 B_2) \oplus (A_2 B_0 A_1 B_1 A_0 B_2 B_0)$$

$$C_5 = A_2 B_0 A_1 B_1 A_0 B_2 B_0$$

Q. 5

(a) $F(A, B, C, D) = \Sigma(1, 3, 5, 8, 10, 14)$

D1, D3, D5, D8, D10, D14 should be connected to *signal 1*, while the left ports (D0, D2, D4, D6, D7, D9, D11, D12, D13, D15) should be connected to *signal 0*.


(b) $F(A, B, C, D) = \Pi(4, 7, 11) = \Sigma(0, 1, 2, 3, 5, 6, 8, 9, 10, 12, 13, 14, 15)$

D4, D7, D11 should be connected to *signal 0*, while the left ports (D0, D1, D2, D3, D5, D6, D8, D9, D10, D12, D13, D14, D15) should be connected to *signal 1*.

Q. 6

Input			Output	
X	Y	B_{in}	Diff	B_{out}
0	0	0	0	0
0	0	1	1	1

0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

2 DIGITAL DESIGN LAB

Task 1

Design File

```

1  `timescale 1ns/1ps
2
3  module decode_74138(
4      input A, B, C,
5      input G1, G2a, G2b,
6      output reg [7:0] Y
7  );
8      always @ * begin
9          if ({G1, G2a, G2b} == 'b100) begin
10             case ({C, B, A})
11                 'd0: Y <= ~'b0000_0001;
12                 'd1: Y <= ~'b0000_0010;
13                 'd2: Y <= ~'b0000_0100;
14                 'd3: Y <= ~'b0000_1000;
15                 'd4: Y <= ~'b0001_0000;
16                 'd5: Y <= ~'b0010_0000;
17                 'd6: Y <= ~'b0100_0000;
18                 'd7: Y <= ~'b1000_0000;
19             endcase
20         end
21         else begin
22             Y = ~'b0000_0000;
23         end
24     end
25 endmodule

```

```
26
27
28 module decode_4_16(
29     input A, B, C, D,
30     input dec_en,
31     output [15:0] Y
32 );
33     reg [2:0] lo_en = 'b000;
34     reg [2:0] hi_en = 'b000;
35     decode_74138 lo(A, B, C, lo_en[2], lo_en[1], lo_en[0], Y[7:0]);
36     decode_74138 hi(A, B, C, hi_en[2], hi_en[1], hi_en[0], Y[15:8]);
37
38     always @ * begin
39         if (dec_en) begin
40             if (!D) begin
41                 lo_en <= 'b100;
42                 hi_en <= 'b000;
43             end
44             else begin
45                 lo_en <= 'b000;
46                 hi_en <= 'b100;
47             end
48         end
49         else begin
50             lo_en <= 'b000;
51             hi_en <= 'b000;
52         end
53     end
54 endmodule
```

Simulation File


```
1 `timescale 1ns/1ps
2
3 module decode_74138_test();
4     reg A, B, C;
5     reg G1, G2a, G2b;
6     wire [7:0] Y;
7
8     decode_74138 dec(A, B, C, G1, G2a, G2b, Y);
9
10    initial begin
11        {G1, G2a, G2b} = 'b000;
12
13        while ({G1, G2a, G2b} < 'b111) begin
14            {C, B, A} = 'b000;
15
16            while ({C, B, A} < 'b111) begin
17                #10 {C, B, A} = {C, B, A} + 1;
18            end
```



```

19         #10 {G1, G2a, G2b} = {G1, G2a, G2b} + 1;
20     end
21     #10 $finish();
22 end
23 endmodule

```

 


The 74138 decoder has three enable ports and should only be enabled when {G1, G2a, G2b} = 'b100, when the decoder is not enabled, no matter what the input is, the output keeps 'b1111_1111. Notice the part of waveform where {G1, G2a, G2b} = 'b100, we have {C, B, A} be the selection signals and the outputs are all as expected.

```

1  `timescale 1ns/1ps
2
3  module decode_4_16_test();
4      reg A, B, C, D;
5      reg dec_en;
6      wire [15:0] Y;
7
8      decode_4_16 dec(A, B, C, D, dec_en, Y);
9
10     initial begin
11         dec_en = 'b0;
12         repeat(2) begin
13             {D, C, B, A} = 'b0000;
14
15             while ({D, C, B, A} < 'b1111) begin
16                 #10 {D, C, B, A} = {D, C, B, A} + 1;
17             end
18
19             #10 dec_en = dec_en + 1;
20         end
21         #10 $finish();
22     end
23 endmodule

```

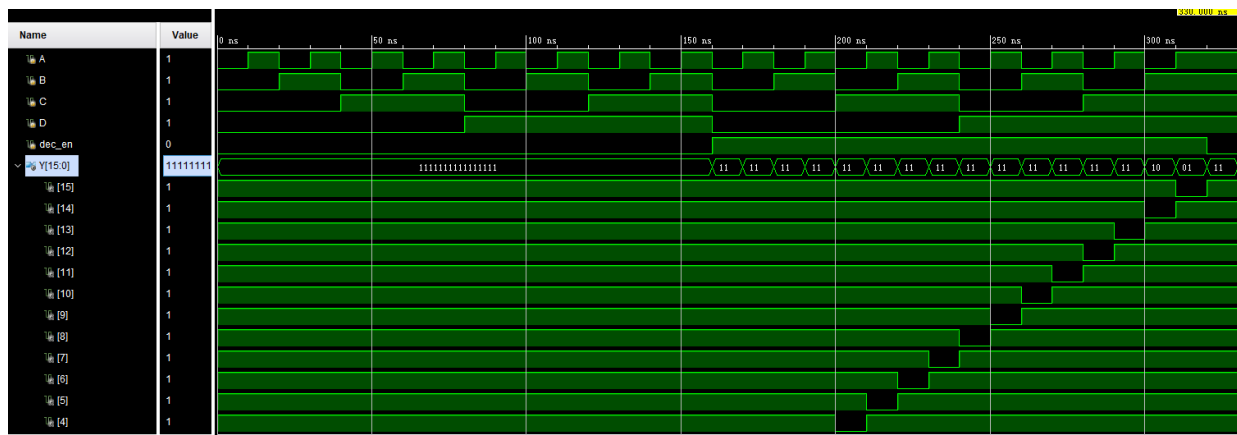

Similarly, when the decoder is not enabled, the output keeps 1111_1111_1111_1111, otherwise it fits the result we expected (one-hot).

Constraint File

```



1  set_property IOSTANDARD LVCMOS33 [get_ports {Y[0]}]
2  set_property IOSTANDARD LVCMOS33 [get_ports {Y[1]}]
3  set_property IOSTANDARD LVCMOS33 [get_ports {Y[2]}]
4  set_property IOSTANDARD LVCMOS33 [get_ports {Y[3]}]
5  set_property IOSTANDARD LVCMOS33 [get_ports {Y[4]}]
6  set_property IOSTANDARD LVCMOS33 [get_ports {Y[5]}]
7  set_property IOSTANDARD LVCMOS33 [get_ports {Y[6]}]
8  set_property IOSTANDARD LVCMOS33 [get_ports {Y[7]}]
9  set_property IOSTANDARD LVCMOS33 [get_ports {Y[8]}]
10 set_property IOSTANDARD LVCMOS33 [get_ports {Y[9]}]
11 set_property IOSTANDARD LVCMOS33 [get_ports {Y[10]}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {Y[11]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {Y[12]}]
14 set_property IOSTANDARD LVCMOS33 [get_ports {Y[13]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {Y[14]}]
16 set_property IOSTANDARD LVCMOS33 [get_ports {Y[15]}]
17 set_property IOSTANDARD LVCMOS33 [get_ports A]
18 set_property IOSTANDARD LVCMOS33 [get_ports B]
19 set_property IOSTANDARD LVCMOS33 [get_ports C]
20 set_property IOSTANDARD LVCMOS33 [get_ports D]
21 set_property IOSTANDARD LVCMOS33 [get_ports dec_en]
22 set_property PACKAGE_PIN U5 [get_ports dec_en]
23 set_property PACKAGE_PIN T5 [get_ports D]
24 set_property PACKAGE_PIN T4 [get_ports C]
25 set_property PACKAGE_PIN R4 [get_ports B]
26 set_property PACKAGE_PIN W4 [get_ports A]
27 set_property PACKAGE_PIN A21 [get_ports {Y[0]}]
28 set_property PACKAGE_PIN E22 [get_ports {Y[1]}]
29 set_property PACKAGE_PIN D22 [get_ports {Y[2]}]
30 set_property PACKAGE_PIN E21 [get_ports {Y[3]}]
31 set_property PACKAGE_PIN D21 [get_ports {Y[4]}]
32 set_property PACKAGE_PIN G21 [get_ports {Y[5]}]
33 set_property PACKAGE_PIN G22 [get_ports {Y[6]}]

```


```

34 set_property PACKAGE_PIN F21 [get_ports {Y[7]}]
35 set_property PACKAGE_PIN J17 [get_ports {Y[8]}]
36 set_property PACKAGE_PIN L14 [get_ports {Y[9]}]
37 set_property PACKAGE_PIN L15 [get_ports {Y[10]}]
38 set_property PACKAGE_PIN L16 [get_ports {Y[11]}]
39 set_property PACKAGE_PIN K16 [get_ports {Y[12]}]
40 set_property PACKAGE_PIN M15 [get_ports {Y[13]}]
41 set_property PACKAGE_PIN M16 [get_ports {Y[14]}]
42 set_property PACKAGE_PIN M17 [get_ports {Y[15]}]


```

  

 
The left fig. shows when decoder is not enabled (the 5th switch counting from right, a.k.a. dec_en is set as 0 now), outputs are all 1. The right one, dec_en = 1, A = B = C = D = 0, then Y[0] acts as the one-hot, since the output ports of 74138 is low-enabled, Y[0] = 0 and the rest 15 bits are 1.



 (a) input as 0101, output as Y[5] = 0, rest are 1;



 (b) input as 0110, output as Y[6] = 0, rest are 1;



(c) input as 0010, output as Y[2] = 0, rest are 1.

Task 2

Design File

```

1 module mux_74151(
2     input mux_en,
3     input s2, s1, s0,
4     input d0, d1, d2, d3, d4, d5, d6, d7,
5     output reg Y,
6     output W

```

```

7 );
8     always @ * begin
9         if (!mux_en) begin
10             case ({s2, s1, s0})
11                 'd0: Y <= d0;
12                 'd1: Y <= d1;
13                 'd2: Y <= d2;
14                 'd3: Y <= d3;
15                 'd4: Y <= d4;
16                 'd5: Y <= d5;
17                 'd6: Y <= d6;
18                 'd7: Y <= d7;
19             endcase
20         end
21         else begin
22             Y <= 'b0;
23         end
24     end
25
26     assign W = ~Y;
27 endmodule

```

As the same of standard 74151, the enable signal is low-enabled, and there should have two output ports, where one is the selected input and the other one is its negation.

```

1 module func_df(
2     input A, B, C, D,
3     output Y
4 );
5     assign Y = (~A & ~B & ~C & ~D) | (B & D) | (A & C) | (~B & C & ~D) | (~A & ~B & ~D);
6 endmodule

```

		AB			
		00	01	11	10
CD	00	1			
	01		1	1	
	11		1	1	1
	10	1		1	1

From the K-map above (actually this is quite similar to checking the truth-table), we conclude:

```

1 case ({A, B, C})
2     'b000: Y = ~D;

```

```

3      'b001: Y = ~D;
4      'b010: Y = D;
5      'b011: Y = D;
6      'b110: Y = D;
7      'b111: Y = 1;
8      'b100: Y = 0;
9      'b101: Y = 1;
10     endcase

```

Thus we map this into our module mux_74151:

```

1  module func_1mux(
2      input A, B, C, D,
3      output Y
4  );
5      mux_74151 mux0(A, B, C,
6                      ~D, ~D, D, D, 0, 1, D, 1,
7                      Y); // we don't use <W>, aka. ~Y
8  endmodule
9
10
11 module func_2mux(
12     input A, B, C, D,
13     output reg Y
14 );
15     reg en1 = 1;
16     reg en2 = 1;
17     wire y1, y2;
18
19     always @ * begin
20         if (D) begin
21             en1 <= 0;
22             en2 <= 1;
23             Y <= y1;
24         end
25         else begin
26             en1 <= 1;
27             en2 <= 0;
28             Y <= y2;
29         end
30     end
31
32     mux_74151 mux1(en1, A, B, C,
33                   0, 0, 1, 1, 0, 1, 1, 1,
34                   y1); // D == 1
35
36     mux_74151 mux2(en2, A, B, C,
37                   1, 1, 0, 0, 0, 1, 0, 1,
38                   y2); // D == 0
39 endmodule


```

Simulation File

```

1  `timescale 1ns/1ps
2
3  module mux_74151_test();
4      reg mux_en;
5      reg s2, s1, s0;
6      reg d0, d1, d2, d3, d4, d5, d6, d7;
7      wire Y, W;
8
9      mux_74151 mux(mux_en,
10                  s2, s1, s0,
11                  d0, d1, d2, d3, d4, d5, d6, d7,
12                  Y, W);
13
14     initial begin
15         mux_en = 'b1;
16         {s2, s1, s0} = 'b000;
17         {d7, d6, d5, d4, d3, d2, d1, d0} = 'b1111_1111;
18
19         #10 mux_en = 'b0;
20         while ({s2, s1, s0} < 'b111) begin
21             #10 {s2, s1, s0} = {s2, s1, s0} + 1;
22             {d7, d6, d5, d4, d3, d2, d1, d0} = 'b0000_0001 << {s2, s1, s0};
23         end
24         #10 $finish();
25     end
26 endmodule

```

 


When testing the mux itself, we just take 1111_1111 as an example input when it is not enabled ($\text{mux_en} == 1$). When it is enabled, since the mux will output the corresponding input $d(x)$ where $x = \{s2, s1, s0\}$, and in the testbench we've let it to be one (while the others be zero), thus the output of mux, Y, should always be 1, and its negation, W, is always 0.

```

1  `timescale 1ns/1ps
2
3  module mux_func_test();
4      reg A, B, C, D,
5      wire Y_df, Y_1mux, Y_2mux;
6
7      func_df df(A, B, C, D, Y_df);
8      func_1mux one_mux(A, B, C, D, Y_1mux);
9      func_2mux two_mux(A, B, C, D, Y_2mux);
10
11     initial begin
12         {A, B, C, D} = 'b0000;
13         while ({A, B, C, D} < 'b1111) begin
14             #10 {A, B, C, D} = {A, B, C, D} + 1;
15         end
16         #10 $finish();
17     end
18 endmodule

```

 

First we notice that three ways to implement the function have the same output, then we check the truth-table and found all the outputs are right.

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1

$$\begin{array}{cccc|c} 1 & 1 & 1 & 1 & 1 \end{array}$$

Problems & Solutions

- (1) At first I couldn't understand why 74138-decoder should has three enable ports, until detailed research *"The three enable pins of chip (in which Two active-low and one active-high) reduce the need for external gates or inverters when expanding."* (Components101, 2018)
- (2) After happening the dilemma that variables went to be X again in the simulation, I have a better understanding of blocking and non-blocking assignments.